

Name - _____

Start time - __ : __

End time - __ : __

For each component listed, provide a brief description of its function:

1. Resistor _____

2. Switch _____

Discuss why it is important to use safety precautions when working with electricity.

Draw a simple diagram illustrating a series circuit and a parallel circuit.

